

Microarchitecture

Computer Architecture



CS3501 – 2024II

PROF.: JGONZALEZ@UTEC.EDU.PE

SRC: HARRIS, HARRIS - DIGITAL DESIGN AND COMPUTER ARCHITECTURE



Executive Summary

2

- **Motivation:** Computer Architecture studies the ISA and Microarchitecture design.
- **Problem:** We need to detail an efficient and simple implementation of the ISA that enables the processor, known as Microarchitecture.
- **Overview:**
 - Definitions of processor microarchitecture and comparison with ISA.
 - Define the ARM single-cycle microarchitecture.
 - Details of the processor datapath and control.
- **Conclusion:** We can build a processor using building blocks to implement an ISA, this defines the microarchitecture.

Outline

3

Introduction

Single Cycle Processor

Datapath


Control

Conclusions

Recall: ISA

4


- The **ISA** is the **interface between** what the **software** commands and what the **hardware** carries out
 - Specifies **how the programmer sees the instructions** to be executed
- The ISA specifies
 - **Memory organization**
 - Address space (ARM: 2^{32} , MIPS: 2^{32})
 - Addressability (ARM: 32 bits, MIPS: 32 bits)
 - Word- or Byte-addressable
 - **Register set**
 - R0 to R15 in ARM
 - 32 registers in MIPS
 - **Instruction set**
 - Opcodes
 - Data types
 - Addressing modes

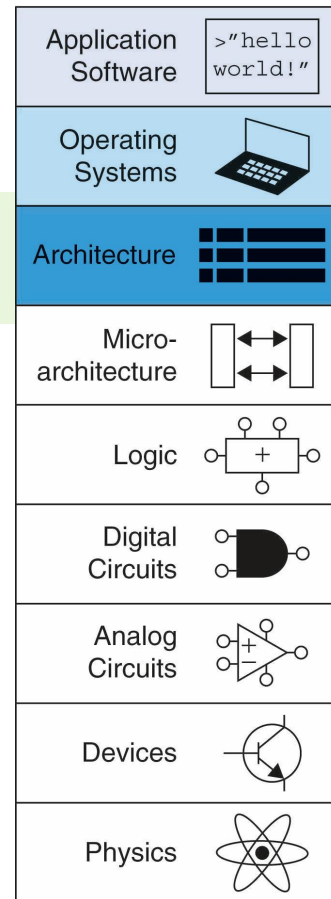

Microarchitecture Definition

5

- **Microarchitecture:** how to implement an architecture in hardware.
 - How the **underlying implementation (invisible to software)** actually executes instructions
 - Microarchitecture can execute instructions in any order **as long as it obeys the semantics specified by the ISA** when making the instruction results **visible to software** (to the programmer).
- **Two main parts in the processor:**
 - **Datapath:** functional blocks
 - **Control:** control signals
- **Multiple implementations** for a single architecture:
 1. **Single-cycle:** Each instruction executes in a single cycle
 2. **Multicycle:** Each instruction is broken up into series of shorter steps
 3. **Pipelined:** Each instruction broken up into series of steps & multiple instructions execute at once

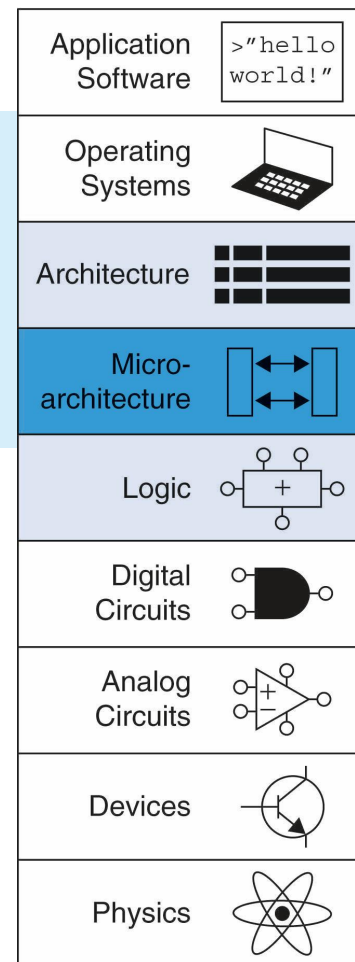

Computer Architecture

6

Computer Architecture = **ISA** + **Microarchitecture**

- All major **Instruction Set Architectures (ISAs)** today are based on the Von-Neumann model.
 - x86, ARM, MIPS, SPARC, Alpha, POWER, RISC-V, ...
- **Microarchitecture (implementation)** can be various as long as it satisfies the specification (ISA)
 - **x86 ISA microarchitectures**: 286, 386, 486, Pentium, Pentium Pro, Pentium 4, Core, Kaby Lake, Coffee Lake, Cascade Lake, Tiger Lake, ...
- **Microarchitecture** usually **changes faster** than **ISA**
 - **Few ISAs** but **many microarchitectures**.
 - In general **Computer Architecture** meets **functional, performance, energy consumption, cost, and other specific goals** (availability, reliability and correctness, Time to Market, Security, safety, predictability, etc.)

ISA vs Microarchitecture

7

ISA:

- Instructions
 - Opcodes, Addressing Modes, Data Types
 - Instruction Types and Formats
 - Registers, Condition Codes
- Memory
 - Address space, Addressability, Alignment
 - Virtual memory management
- Call, Interrupt/Exception Handling
- Access Control, Priority/Privilege
- I/O: memory-mapped vs. instr.
- Task/thread Management
- Power and Thermal Management
- Multi-threading support, Multiprocessor support



Intel® 64 and IA-32 Architectures
Software Developer's Manual

Volume 1:
Basic Architecture

Microarchitecture:

- **Implementation of the ISA** under specific design constraints and goals
- **Anything done in hardware** without exposure to software
 - Pipelining
 - In-order versus out-of-order instruction execution
 - Memory access scheduling policy
 - Speculative execution
 - Superscalar processing (multiple instruction issue?)
 - Clock gating
 - Caching? Levels, size, associativity, replacement policy
 - Prefetching?
 - Voltage/frequency scaling?
 - Error correction?



Processor Performance

8

Different microarchitectures, different performance

- Program execution time

$$\text{Execution Time} = (\# \text{instructions}) (\text{cycles/instruction}) (\text{seconds/cycle})$$

- **Definitions:**

- CPI: Cycles/instruction
- clock period: seconds/cycle
- IPC: instructions/cycle = IPC

- **Challenge is to satisfy constraints of:**

- Cost
- Power
- Performance

More about performance, later in lecture.

Outline

9

Introduction

Single Cycle Processor

Datapath

Control

Conclusions

Single Cycle Processor

10

- Each instruction takes a single clock cycle to execute
- **Execution** with only combinational logic is used to implement instruction execution
 - No intermediate invisible state updates.

AS = Architectural state


at the beginning of a clock cycle (programmer visible)




Process instruction in one clock cycle
(programmer invisible)



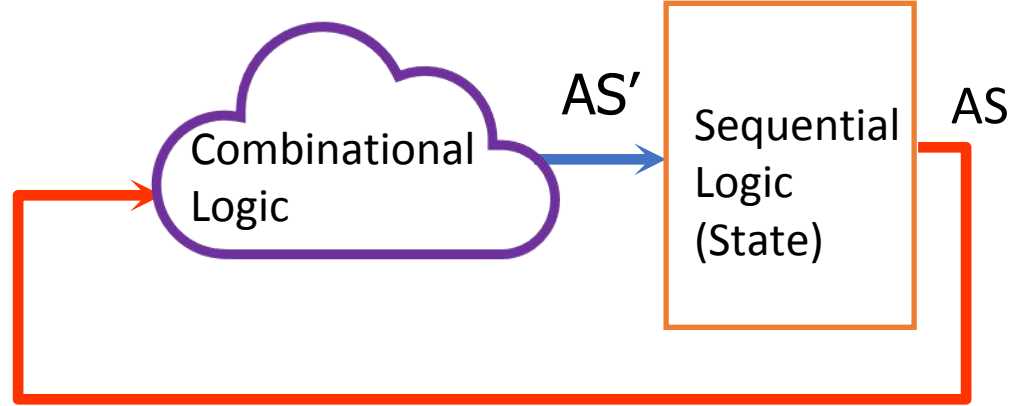AS' = Architectural state
at the end of a clock cycle
(programmer visible)




Single-Cycle ARM Processor

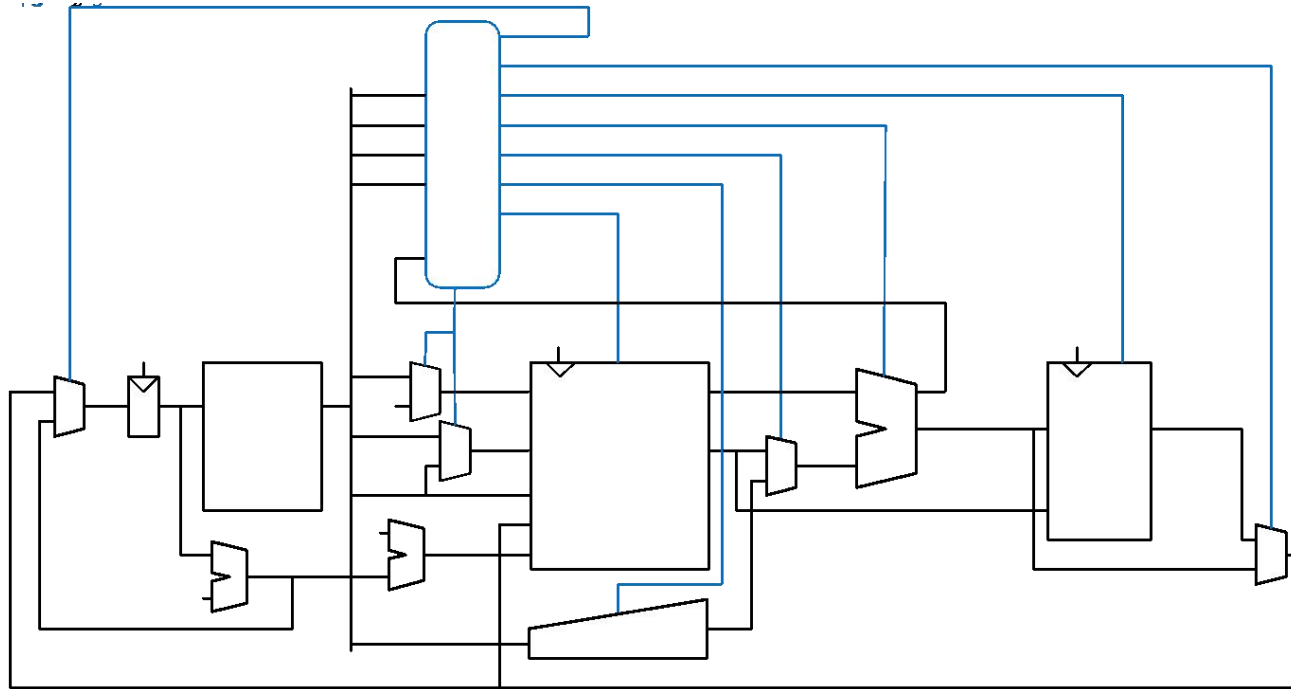

In this lecture, we analyze the single-cycle ARM processor.

Architectural State Elements

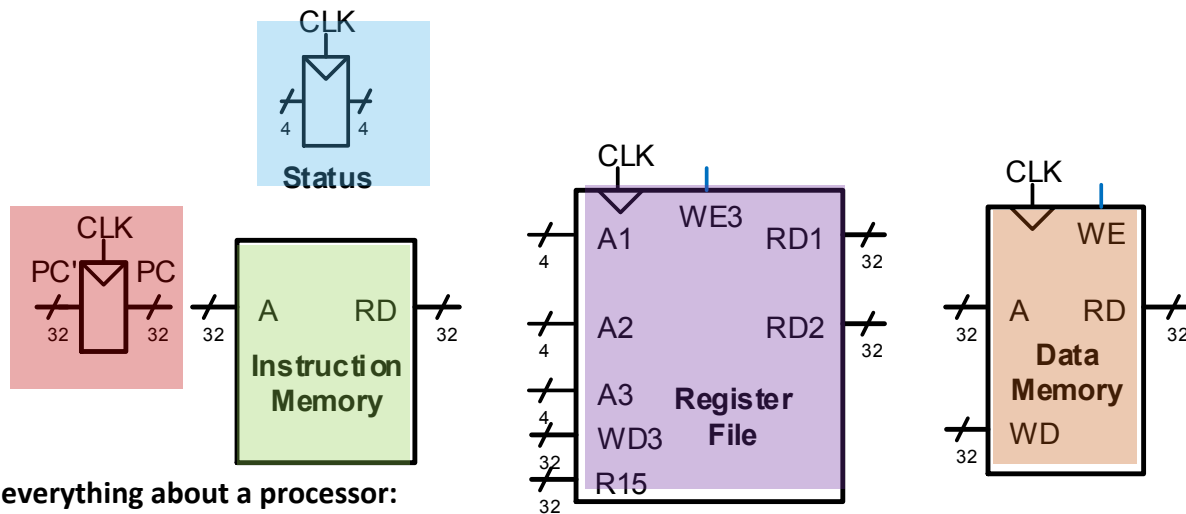

Determines everything about a processor:

- **Program counter:** 32-bit register
- **Status register:** 4-bit register. Also known as CPSR for flags: interrupt, overflow, carry, zero, negative, etc.
- **Instruction memory:** Takes input 32-bit address A and reads the 32-bit data (i.e., instruction) from that address to the read data output RD.
- **Register file:** The 16 register (including PC), 32-bit register file has 2 read ports and 1 write port
- **Data memory:** Has a single read/write port. If the write enable, WE, is 1, it writes data WD into address A on the rising edge of the clock. If the write enable is 0, it reads address A onto RD.

Outline

13

Introduction

Single Cycle Processor

Datapath

Control

Conclusions

ARM Single-Cycle Processor Evaluation

14

- Consider **subset** of ARM instructions:
 - **Memory instructions:**
 - **LDR, STR**
 - with **positive** immediate offset
 - **Data-processing instructions:**
 - **ADD, SUB, AND, ORR**
 - with register and immediate Src2, but **no shifts**
 - **Branch instructions:**
 - **B**

In this lecture, we analyze the single-cycle ARM processor.

LDR Instruction


15

- **Datapath:** start with LDR instruction

- **Example:**


LDR R1, [R2, #5]

LDR Rd, [Rn, imm12]

 

Single-Cycle Datapath: LDR fetch



STEP 1: Fetch instruction

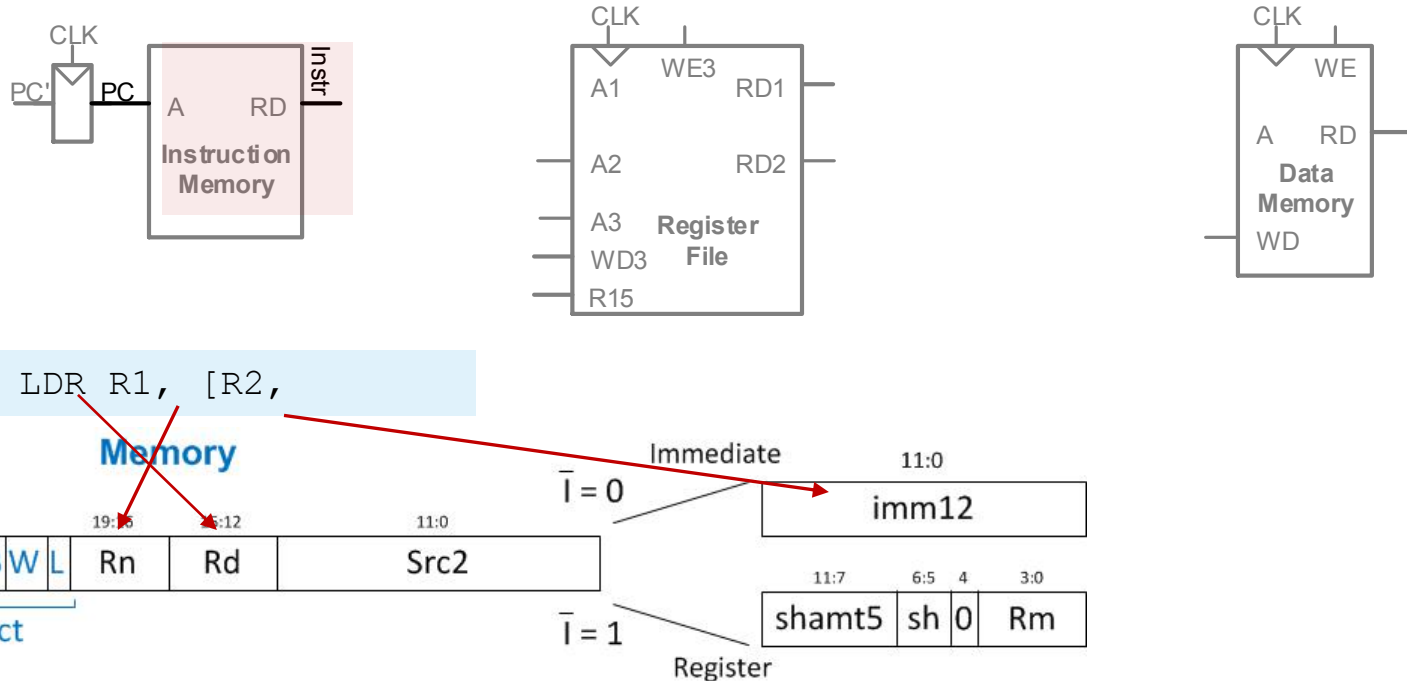

Single-Cycle Datapath: LDR Reg Read

17


STEP 2: Read source operands from RF

 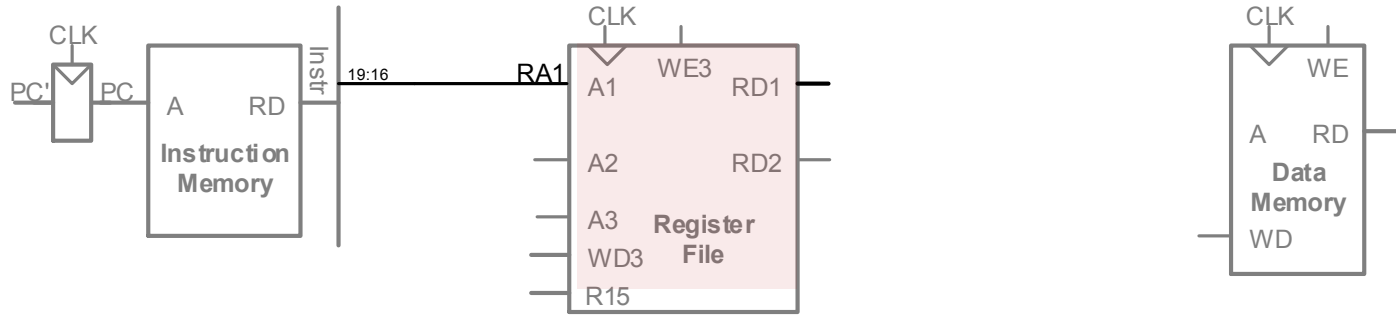

Single-Cycle Datapath: LDR Immediate

18


STEP 3: Extend the immediate

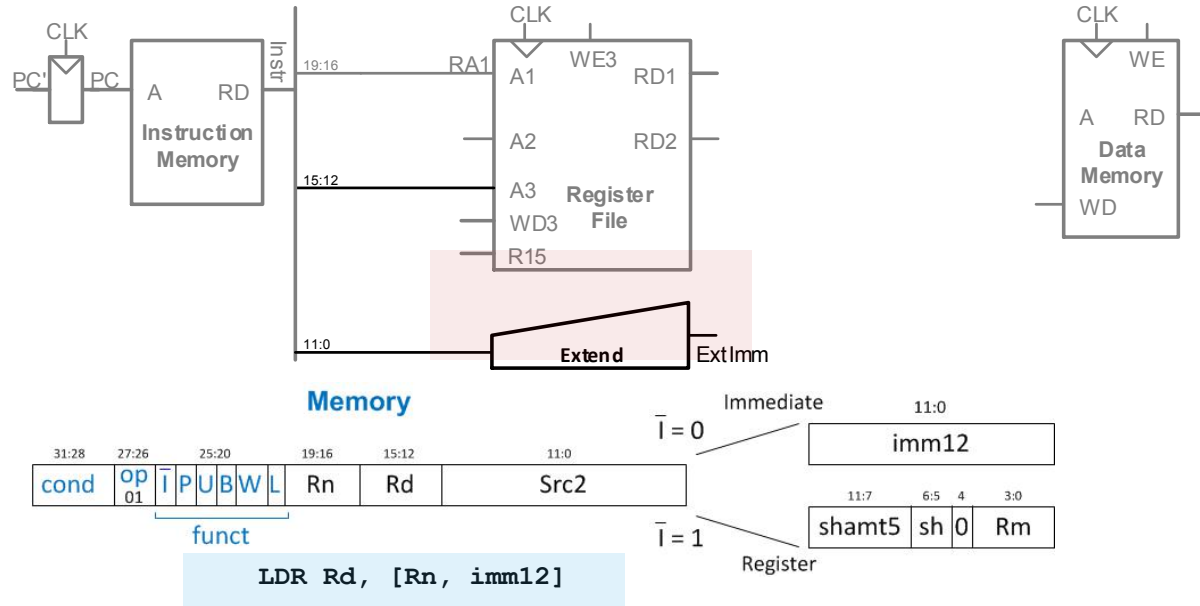

Single-Cycle Datapath: LDR Address

19



STEP 4: Compute the memory address

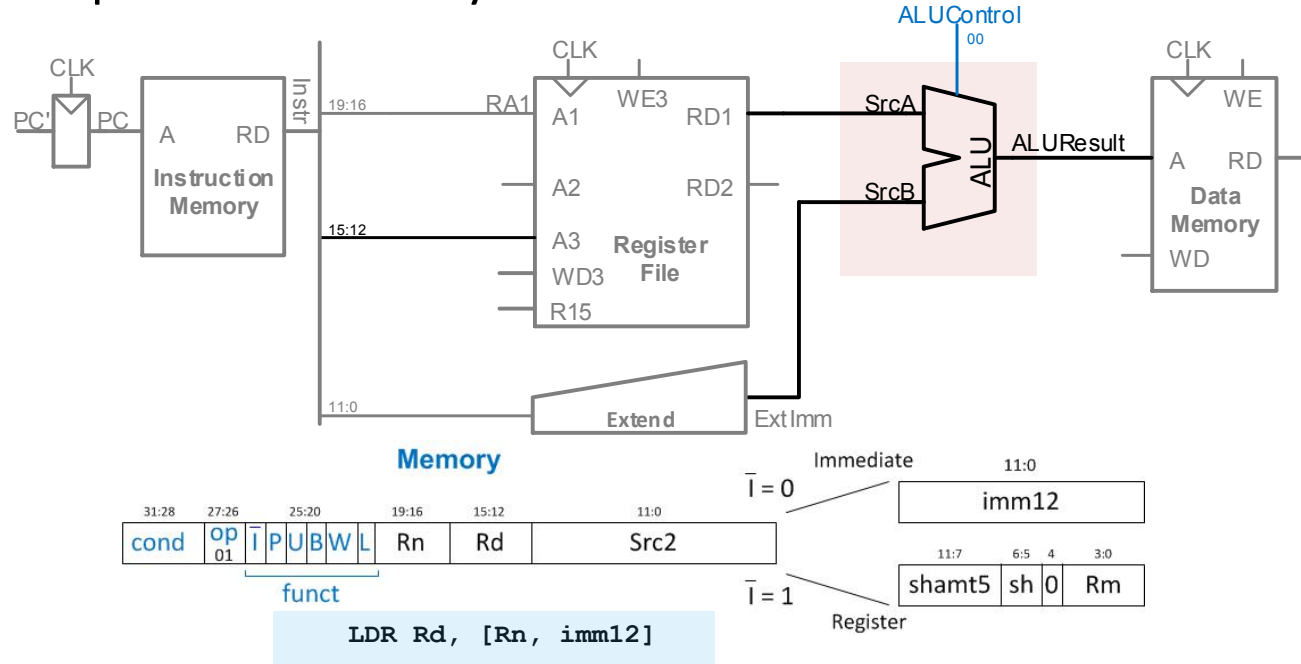

Single-Cycle Datapath: LDR Mem Read

20

 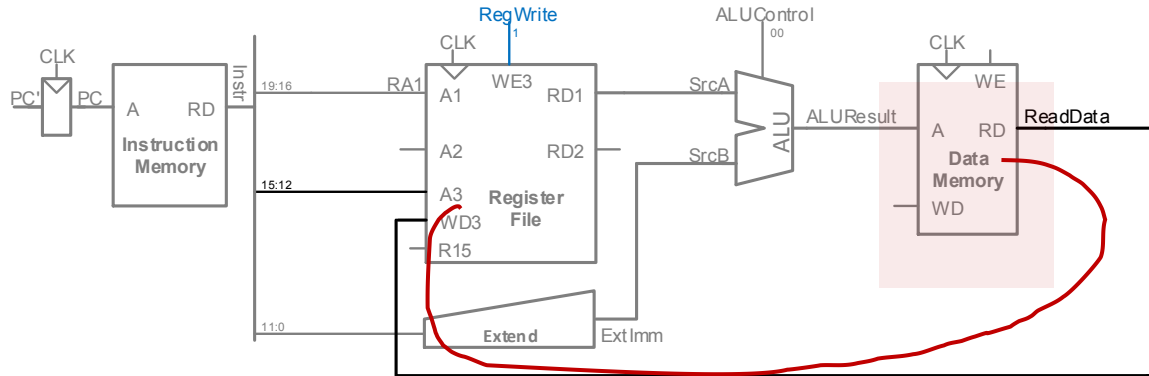
STEP 5: Read data from memory and write it back to register file



Single-Cycle Datapath: PC Increment

21

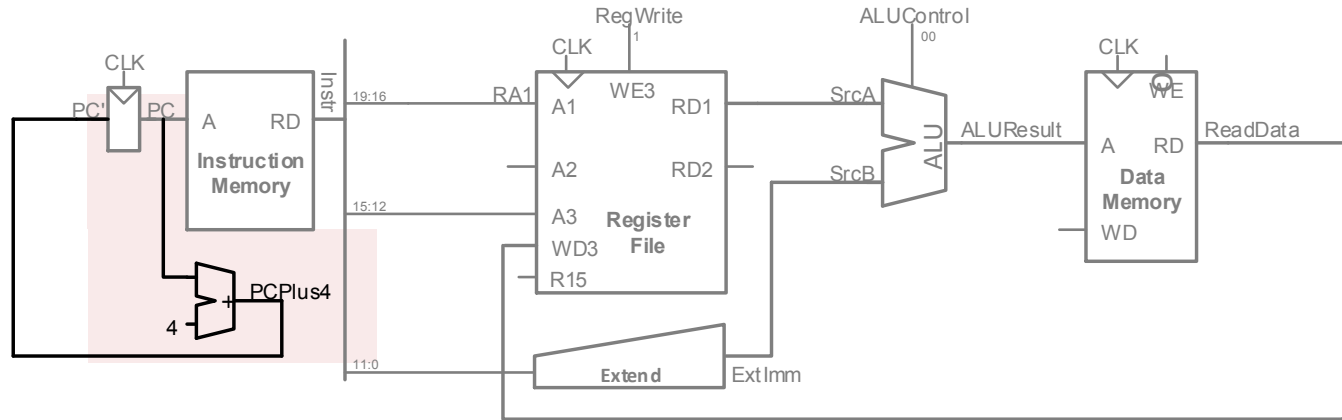STEP 6: Determine address of next instruction




Single-Cycle Datapath: Access to PC

22

PC can be source/destination of instruction

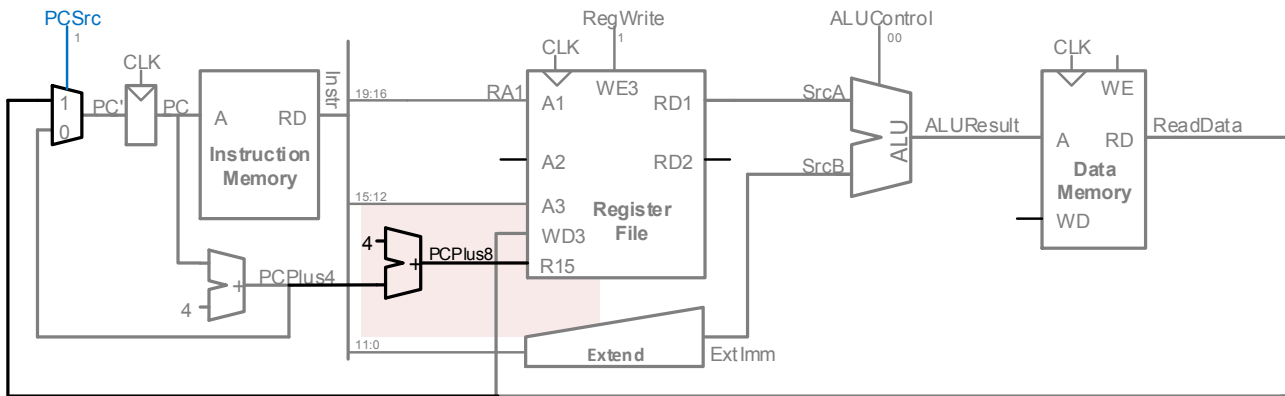- **Source:** R15 must be available in Register File
 - **PC** is read as the current **PC plus 8**
- **Destination:** Be able to write result to PC




- This is because **older ARM processors always fetched two instructions ahead** of the currently executed instructions.
- The reason **ARM retains this definition is to ensure compatibility with earlier processors.**

Single-Cycle Datapath: STR

23

Expand datapath to handle STR:

- Write data in Rd to memory


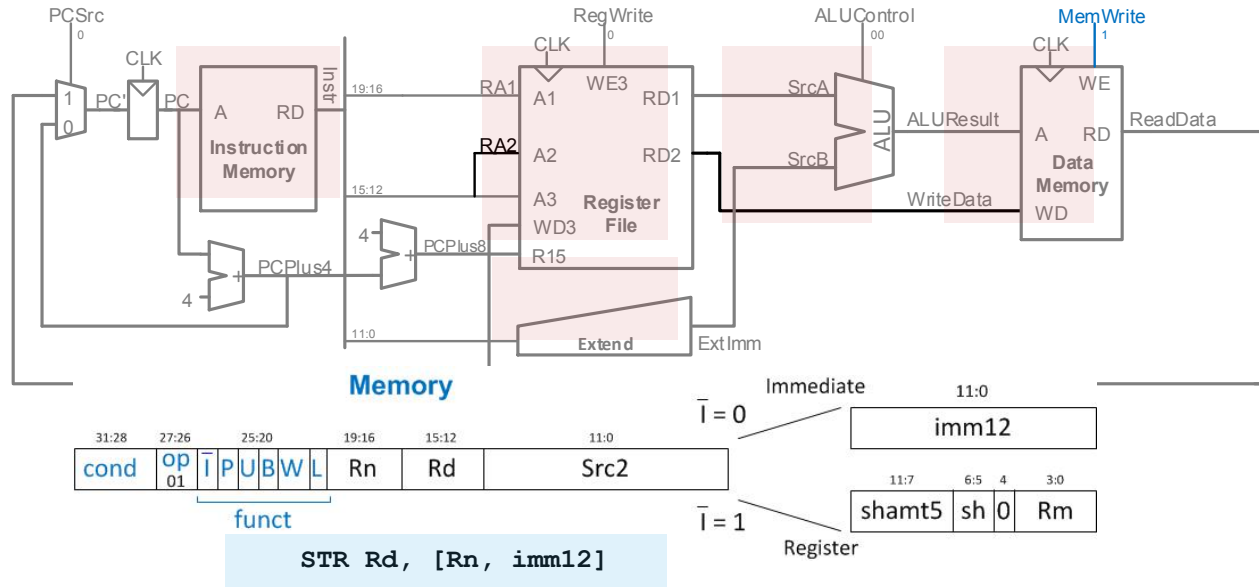


Single-Cycle Datapath: Data-processing

24

With **immediate** Src2:

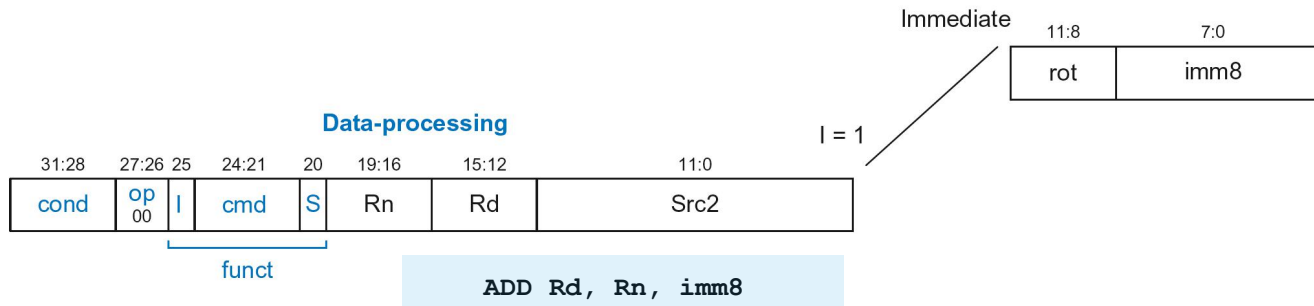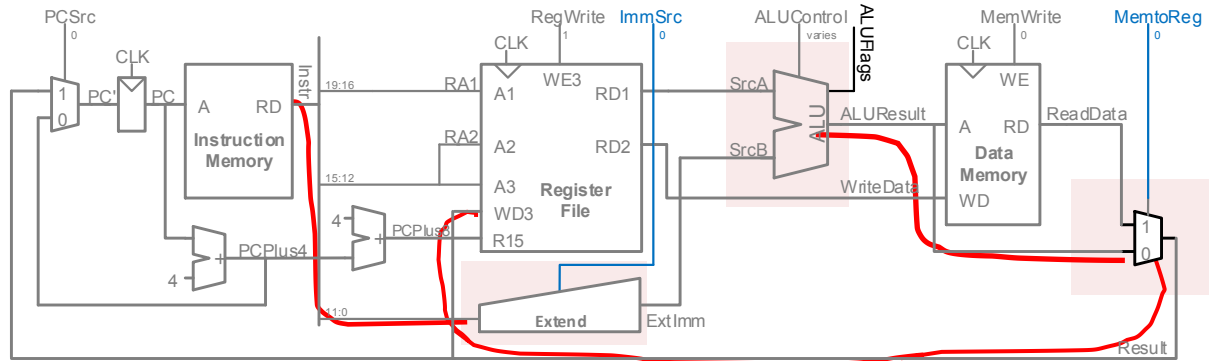- Read from Rn and Imm8
(*ImmSrc* chooses the zero-extended Imm8 instead of Imm12)
- Write *ALUResult* to register file
- Write to Rd





Single-Cycle Datapath: Data-processing

25

With **register Src2**:

  - Read from R_n and R_m (instead of $Imm8$)
- Write *ALUResult* to register file
- Write to R_d




ADD R_d, R_n, R_m

Single-Cycle Datapath: Data-processing

26

With **register** Src2:

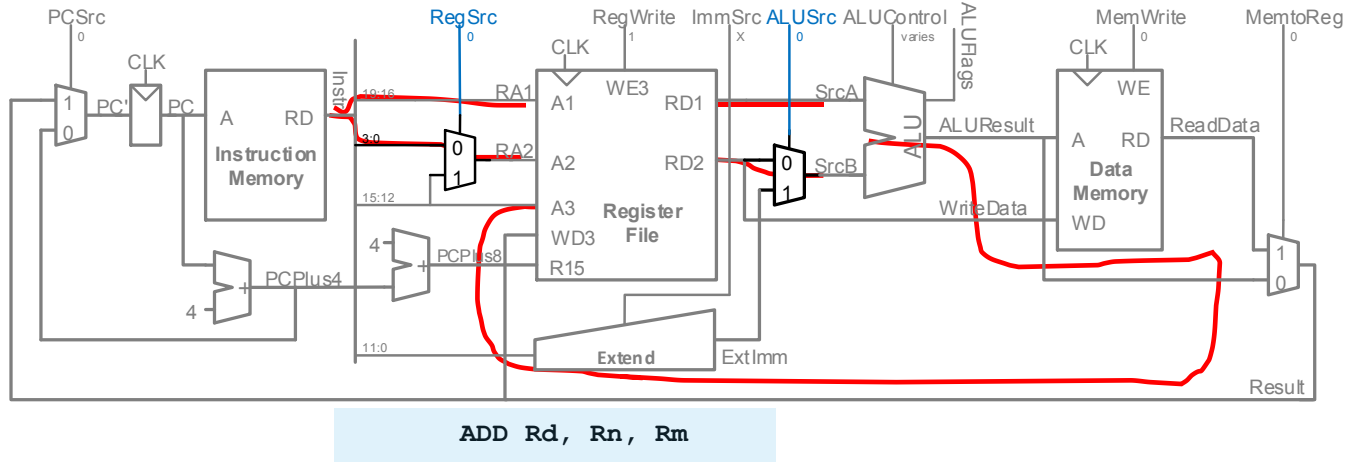- Read from Rn and Rm (instead of Imm8)
- Write *ALUResult* to register file
- Write to Rd





Single-Cycle Datapath: B

Calculate branch target address:


$$BTA = (ExtImm) + (PC + 8)$$

$ExtImm = Imm24 \ll 2$ and sign-extended

 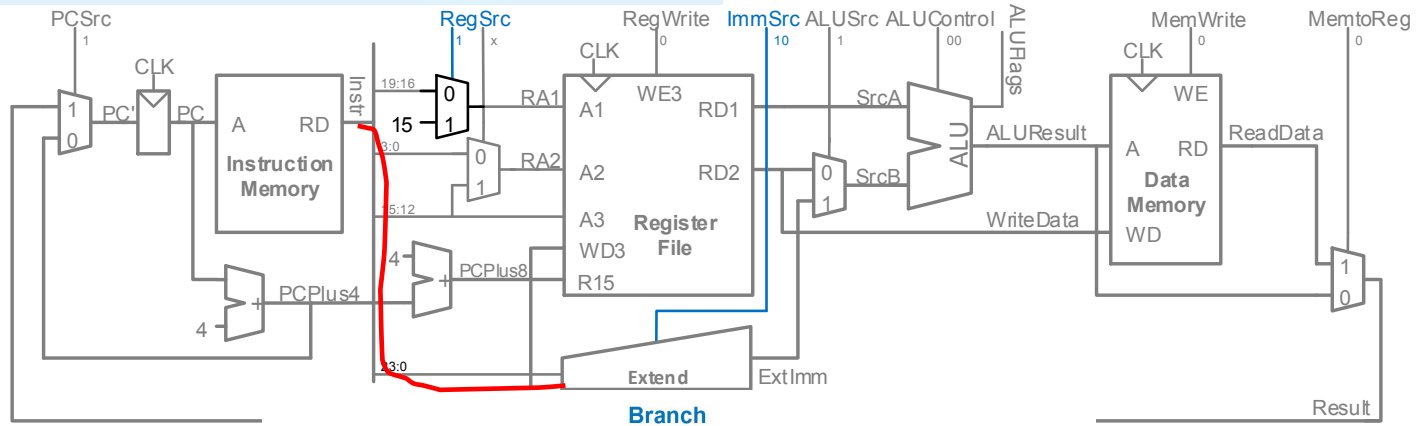

Single-Cycle Datapath: ExtImm


28

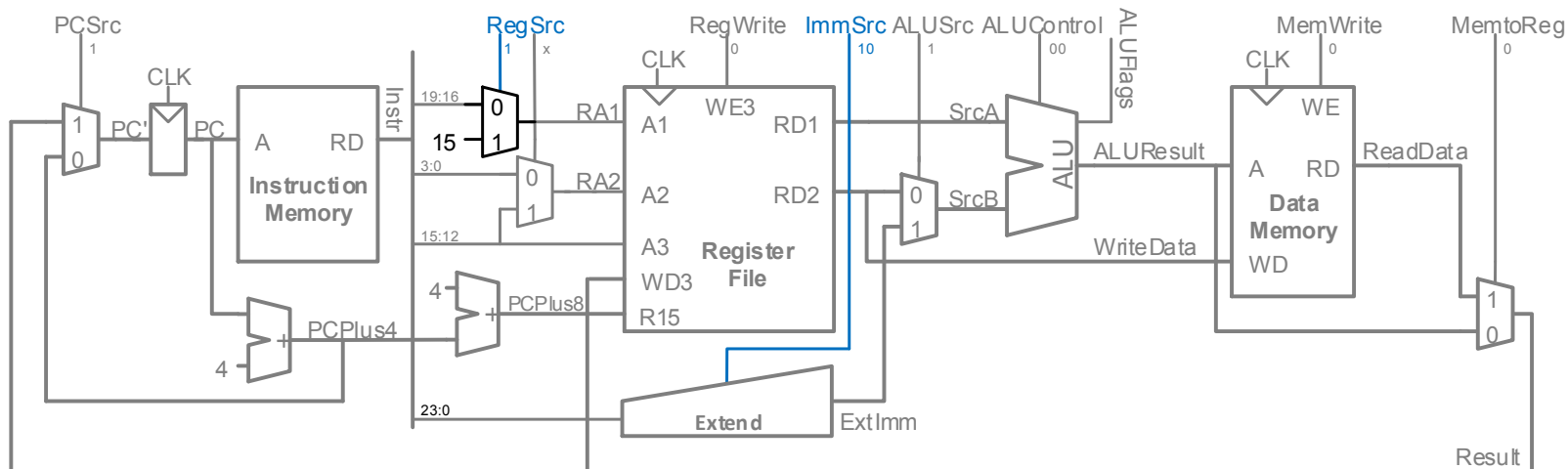

ImmSrc _{1:0}	ExtImm	Description
00	{24'b0, Instr _{7:0} }	Zero-extended <i>imm8</i>
01	{20'b0, Instr _{11:0} }	Zero-extended <i>imm12</i>
10	{6{Instr ₂₃ }, Instr _{23:0} }	Sign-extended <i>imm24</i>

Single-Cycle ARM Processor

29

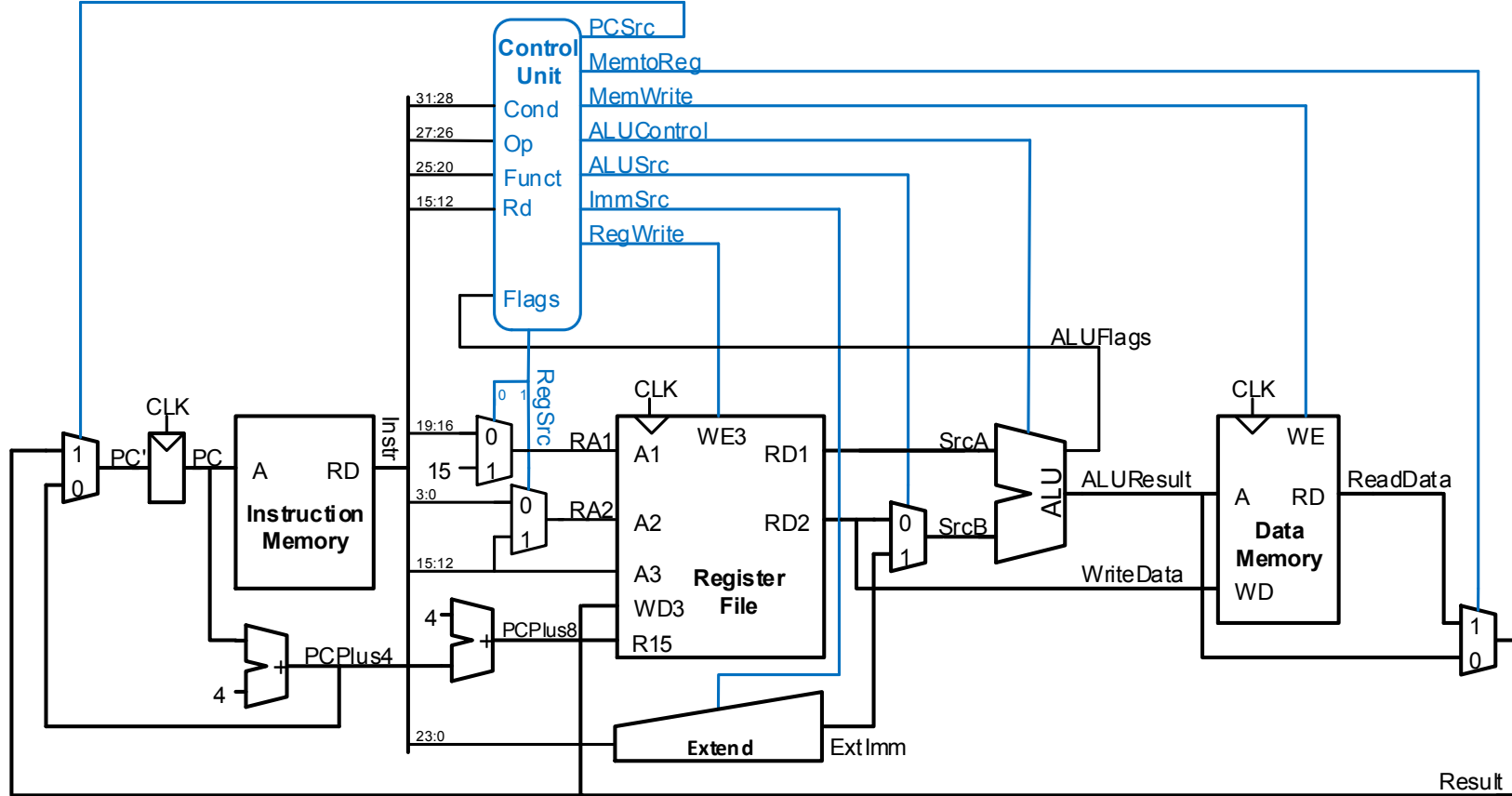

Outline

30

Introduction

Single Cycle Processor


Datapath

Control

Conclusions


Single-Cycle Control

31

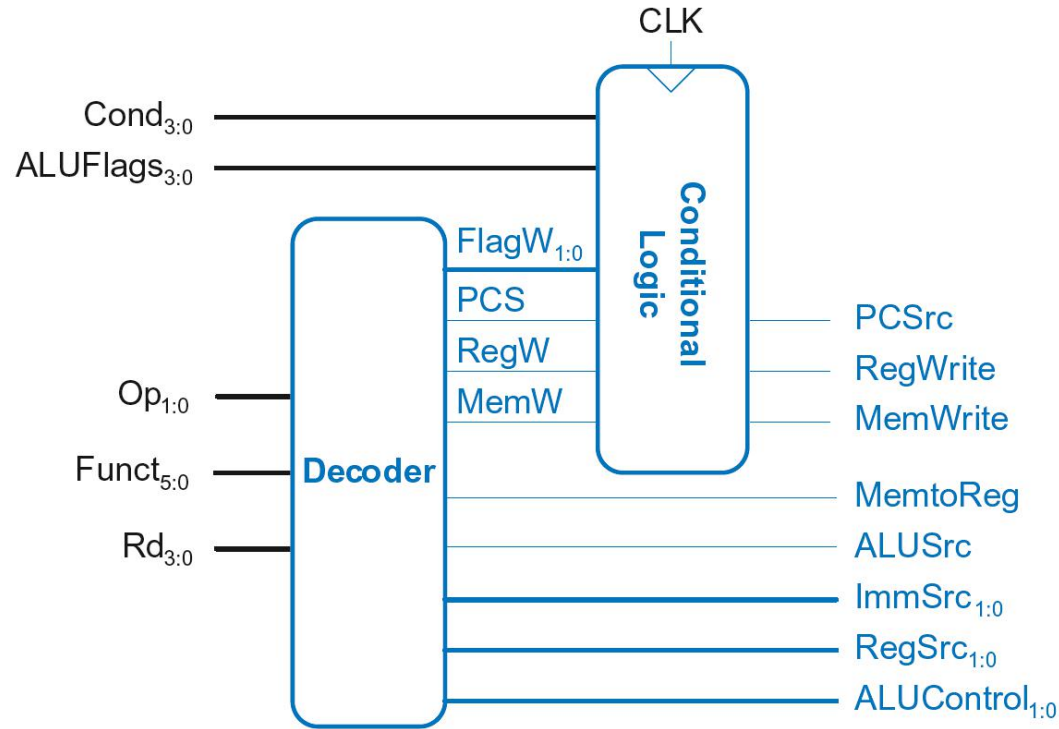


Single-Cycle ARM Processor

32

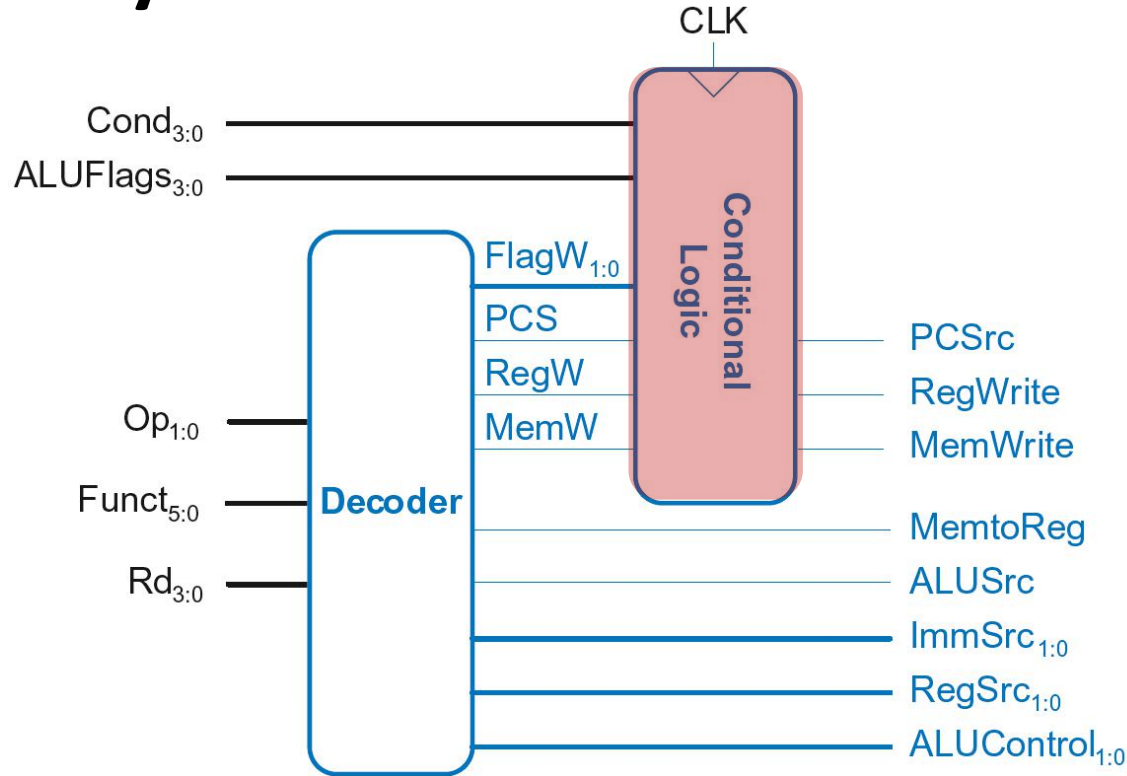


Single-Cycle Control: Signals

33

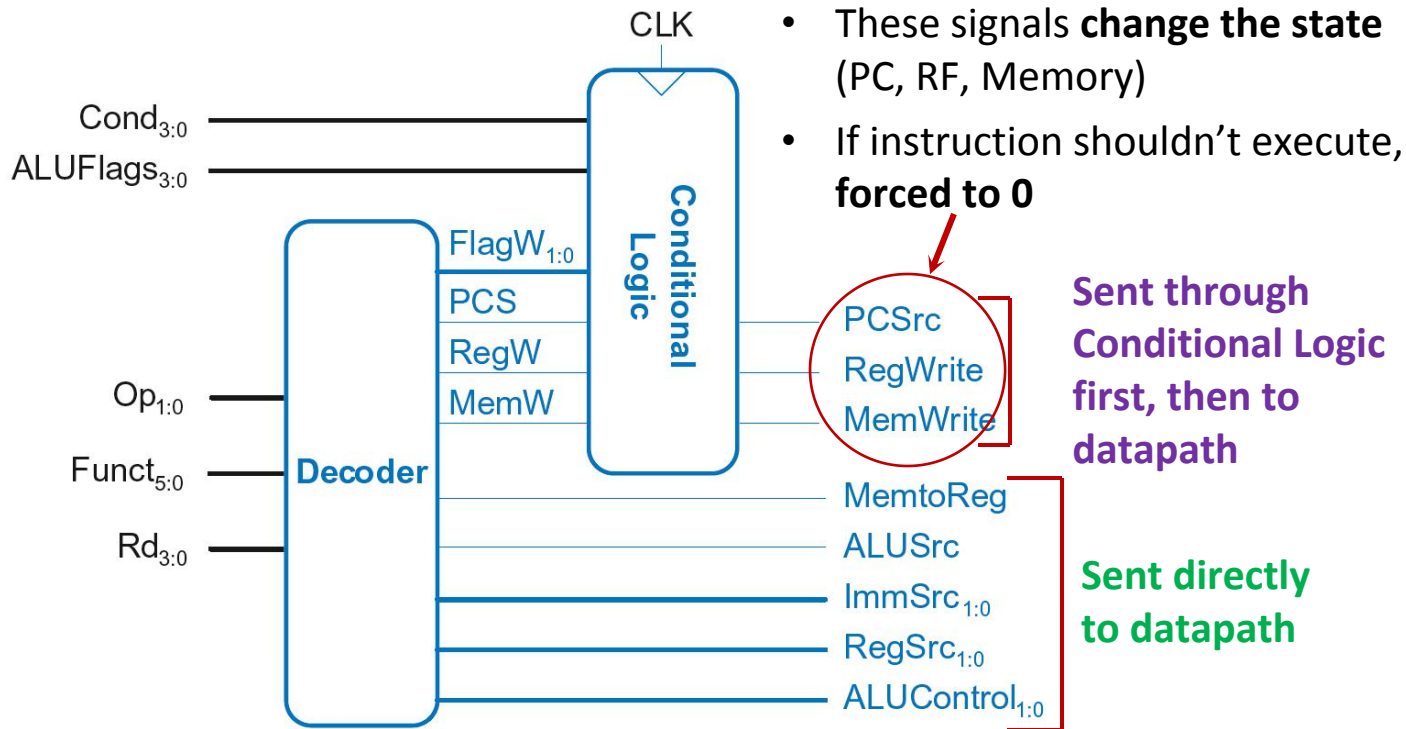

Single-Cycle Control: Signals


34

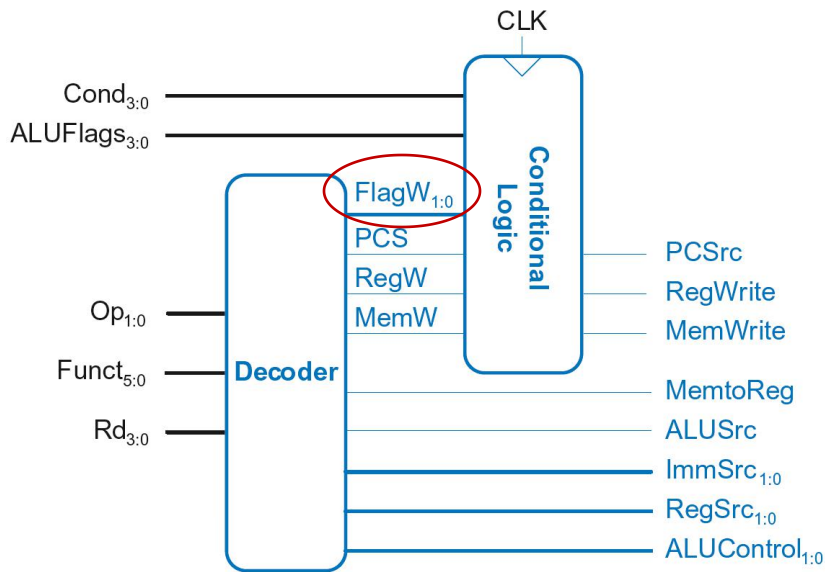

- **$FlagW_{1:0}$** : Flag Write signal, asserted when $ALUFlags$ should be saved (i.e., on instruction with $S=1$)
- ADD, SUB update all flags (**NZCV**)
- AND, ORR only update **NZ** flags
- So, two bits needed:
 - $FlagW_1 = 1$** : NZ saved ($ALUFlags_{3:2}$ saved)
 - $FlagW_0 = 1$** : CV saved ($ALUFlags_{1:0}$ saved)

Single-Cycle Control: Decoder

35

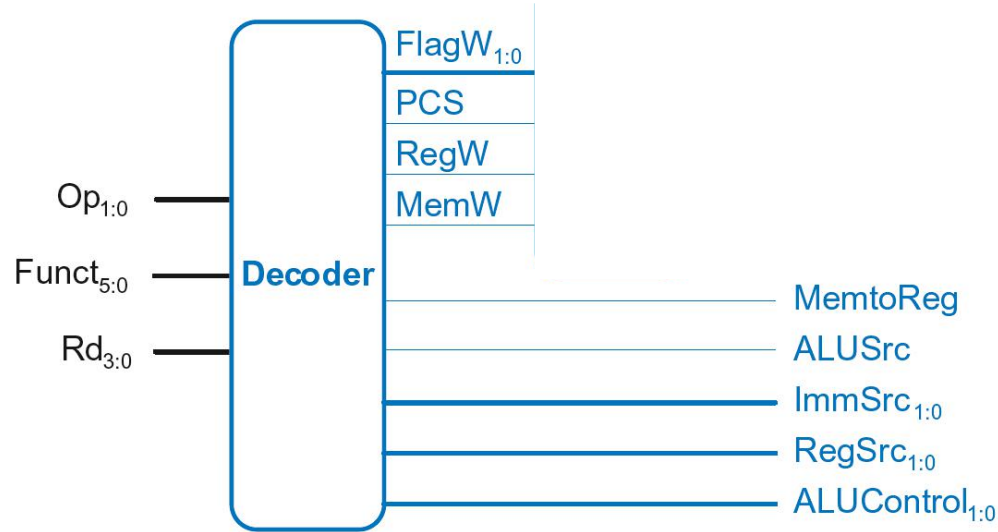


Single-Cycle Control: Decoder

36

Submodules:

- Main Decoder
- ALU Decoder
- PC Logic

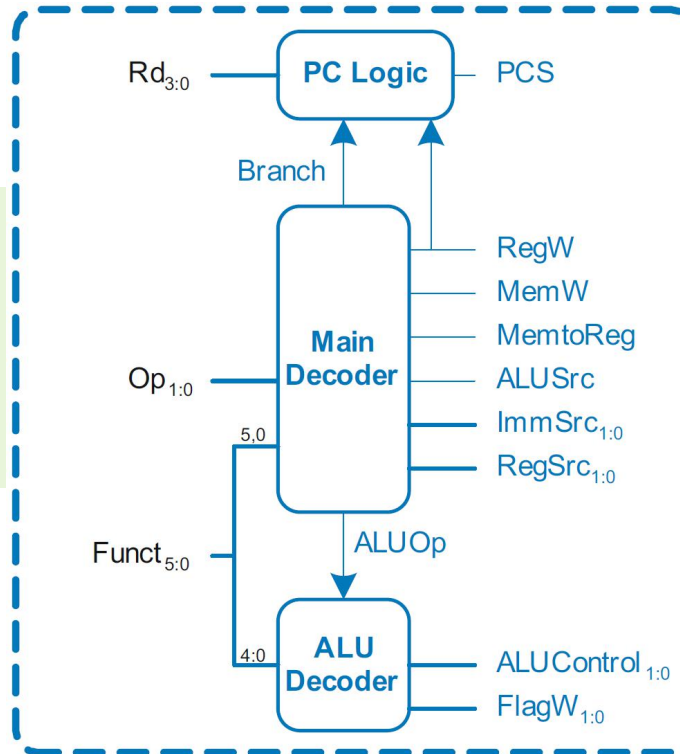


Control Unit: Main Decoder

37

Op	Funct ₅	Funct ₀	Type	Branch	MemtoReg	MemW	ALUSrc	ImmSrc	RegW	RegSrc	ALUOp
00	0	X	DP Reg	0	0	0	0	XX	1	00	1
00	1	X	DP Imm	0	0	0	1	00	1	X0	1
01	X	0	STR	0	X	1	1	01	0	10	0
01	X	1	LDR	0	1	0	1	01	1	X0	0
11	X	X	B	1	0	0	1	10	0	X1	0

Recall: ALU

38

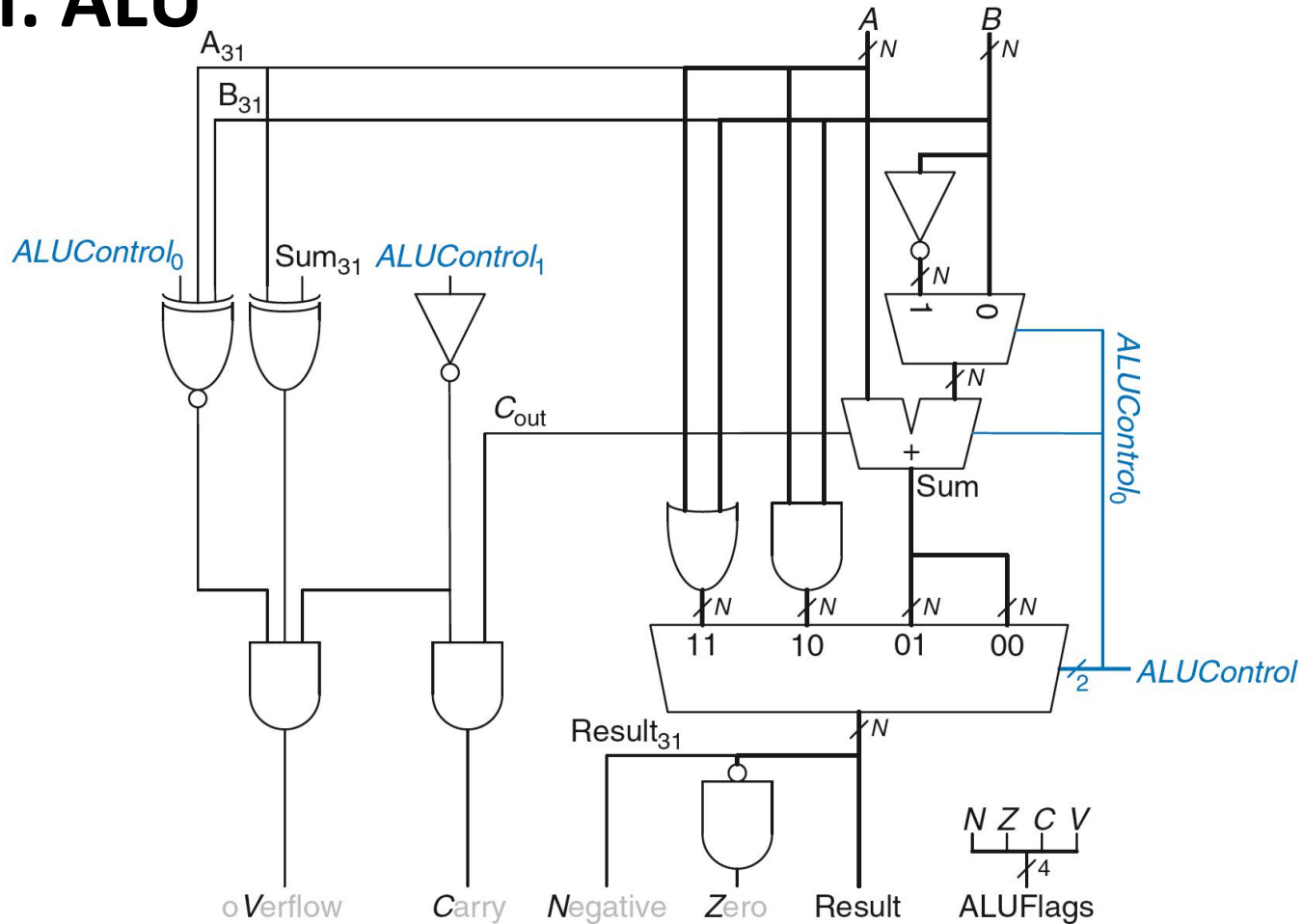

Control Unit: ALU Decoder

39

ALUOp	Funct _{4:1} (cmd)	Funct ₀ (S)	Type	ALUControl _{1:0}	FlagW _{1:0}
0	X	X	Not DP	00	00
1	0100	0	ADD	00	00
		1			11
	0010	0	SUB	01	00
		1			11
	0000	0	AND	10	00
		1			10
	1100	0	ORR	11	00
		1			10


- **FlagW₁** = 1: NZ (*Flags_{3:2}*) should be saved
- **FlagW₀** = 1: CV (*Flags_{1:0}*) should be saved

Single-Cycle Control: PC Logic

40

$PCS = 1$ if PC is written by an instruction or branch (B):
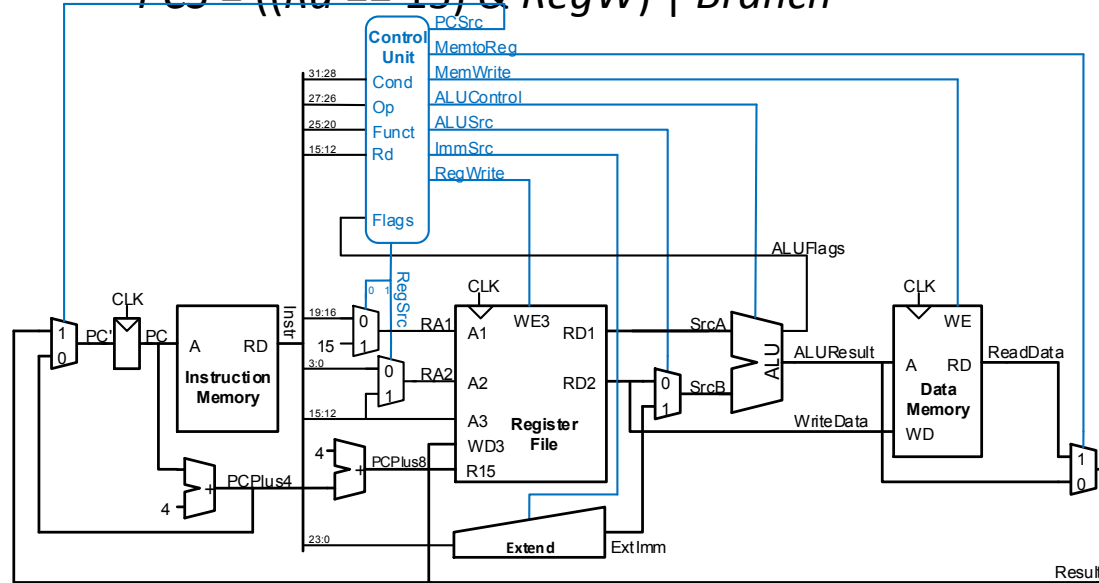
$$PCS = ((Rd == 15) \& RegW) \mid Branch$$




If instruction is executed: $PCSrc = PCS$

Else: $PCSrc = 0$ (i.e., $PC = PC + 4$)

Conditional Logic

41

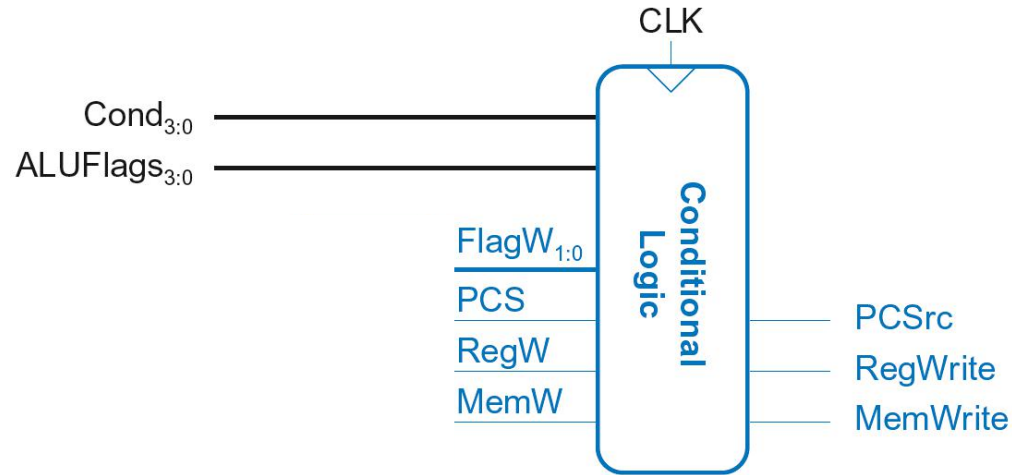


Function:

1. **Check if instruction should execute** (if not, force $PCSrc$, $RegWrite$, and $MemWrite$ to 0)
2. Possibly update Status Register ($Flags_{3:0}$)

Conditional Logic: Conditional Execution

42

Flags_{3:0} is the
status register

 

Depending on condition mnemonic (**Cond_{3:0}**) and condition flags (**Flags_{3:0}**) the instruction is executed (**CondEx = 1**)

Recall: Condition Mnemonics


43

Cond _{3:0}	Mnemonic	Name	CondEx
0000	EQ	Equal	
0001	NE	Not equal	
0010	CS / HS	Carry set / Unsigned higher or same	
0011	CC / LO	Carry clear / Unsigned lower	
0100	MI	Minus / Negative	
0101	PL	Plus / Positive of zero	
0110	VS	Overflow / Overflow set	
0111	VC	No overflow / Overflow clear	
1000	HI	Unsigned higher	
1001	LS	Unsigned lower or same	
1010	GE	Signed greater than or equal	
1011	LT	Signed less than	
1100	GT	Signed greater than	
1101	LE	Signed less than or equal	
1110	AL (or none)	Always / unconditional	ignored

Example: Conditional Execution

44

Flags_{3:0} =
NZCV

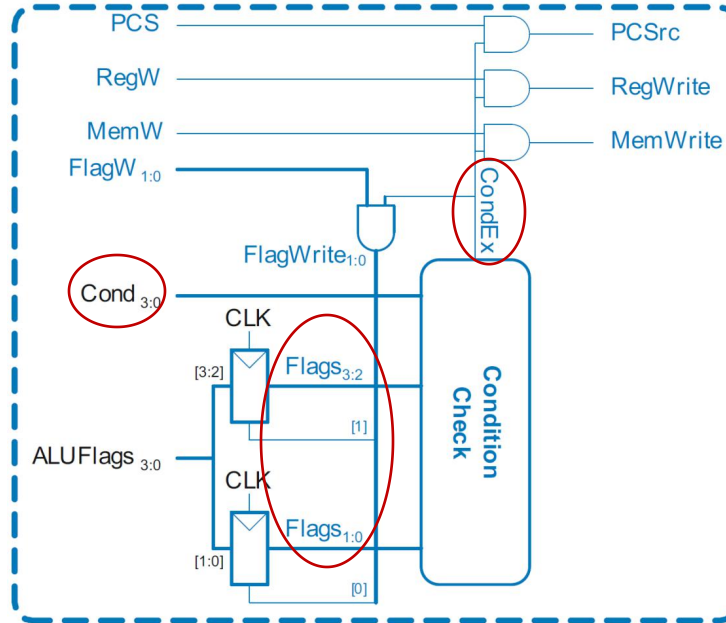


Example: AND R1, R2, R3

Cond_{3:0}=1110 (unconditional) => CondEx = 1

Example: Conditional Execution

Flags_{3:0} =
NZCV

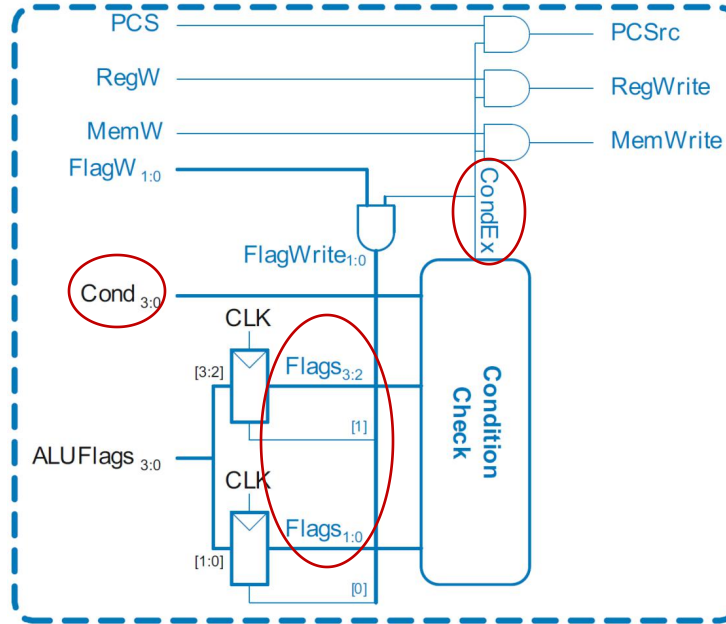


Example: EOREQ R5, R6, R7

Cond_{3:0}=0000 (EQ): if **Flags_{3:2}=0100** => **CondEx = 1**

Conditional Logic

46

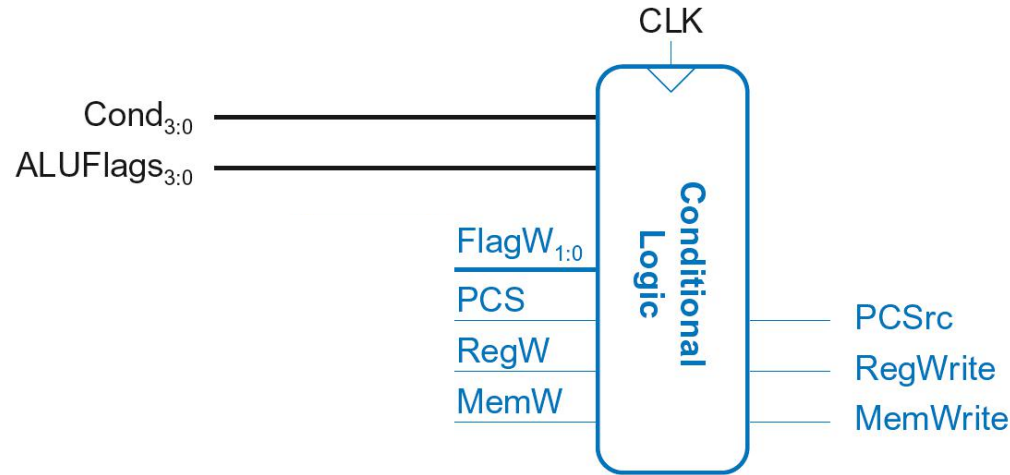


Function:

1. Check if instruction should execute (if not, force PCSrc, RegWrite, and MemWrite to 0)
2. **Possibly update Status Register (Flags_{3:0})**

Conditional Logic: Update (Set) Flags

47


Flags_{3:0} =
NZCV

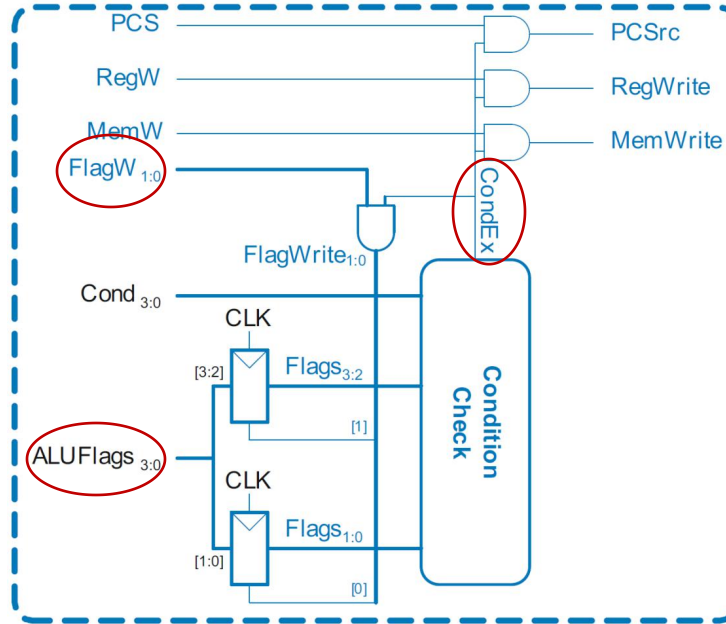

Flags_{3:0} **updated** (with ALUFlags_{3:0}) if:

- **FlagW** is 1 (i.e., the instruction's S-bit is 1) AND
- **CondEx** is 1 (the instruction should be executed)

Conditional Logic: Update (Set) Flags

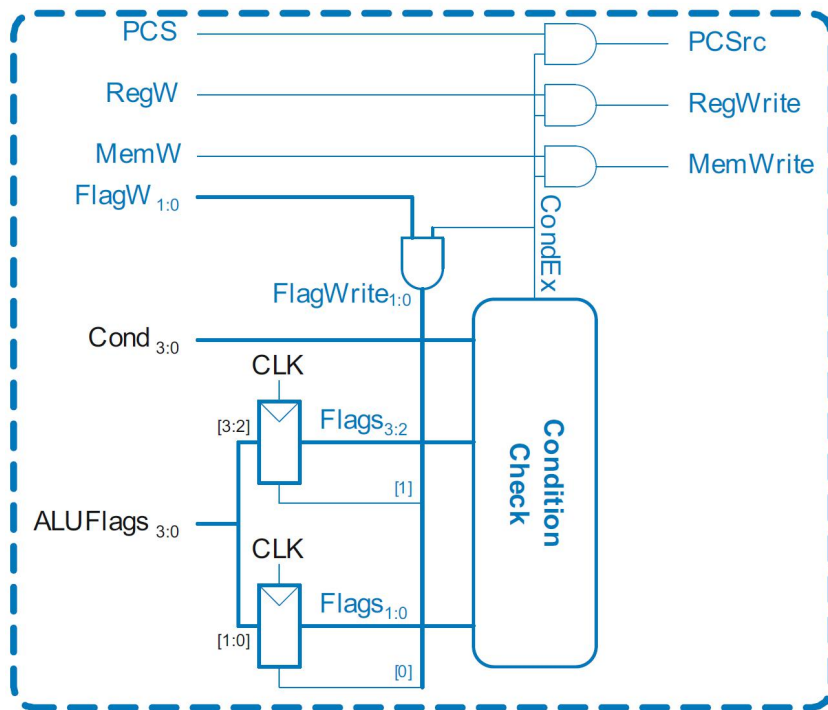

Recall:

- ADD, SUB update **all** Flags
- AND, OR update **NZ only**
- So Flags status register has two write enables: **FlagW_{1:0}**

Recall: ALU Decoder

49


ALUOp	Funct _{4:1} (cmd)	Funct ₀ (S)	Type	ALUControl _{1:0}	FlagW _{1:0}
0	X	X	Not DP	00	00
1	0100	0	ADD	00	00
		1			11
	0010	0	SUB	01	00
		1			11
	0000	0	AND	10	00
		1			10
	1100	0	ORR	11	00
		1			10

- **FlagW₁** = 1: NZ (*Flags*_{3:2}) should be saved
- **FlagW₀** = 1: CV (*Flags*_{1:0}) should be saved

Example: Update (Set) Flags

50

All Flags
updated

 

Example: SUBS R5, R6, R7


FlagW_{1:0} = 11 AND CondEx = 1 (unconditional) => FlagWrite_{1:0} = 11

Example: Update (Set) Flags

51

Flags_{3:0} = NZCV

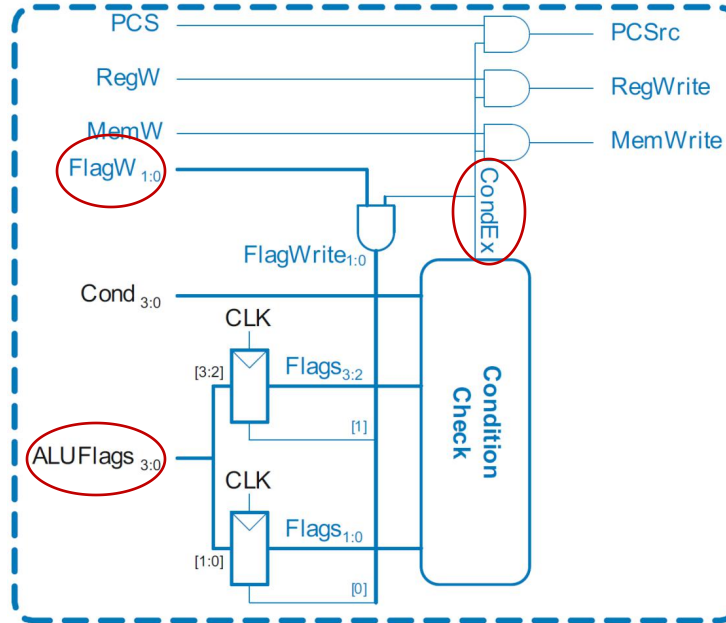- Only **Flags_{3:2}** updated
- i.e., only **NZ** Flags updated




Example: ANDS R7, R1, R3

FlagW_{1:0} = 10 AND CondEx = 1 (unconditional) => FlagWrite_{1:0} = 10

Example: ORR


52

Op	Func	Func	Type	B	Me	Me	ALU	ImmS	Reg	RegS	ALU
	5	0					Src	rc		rc	pc

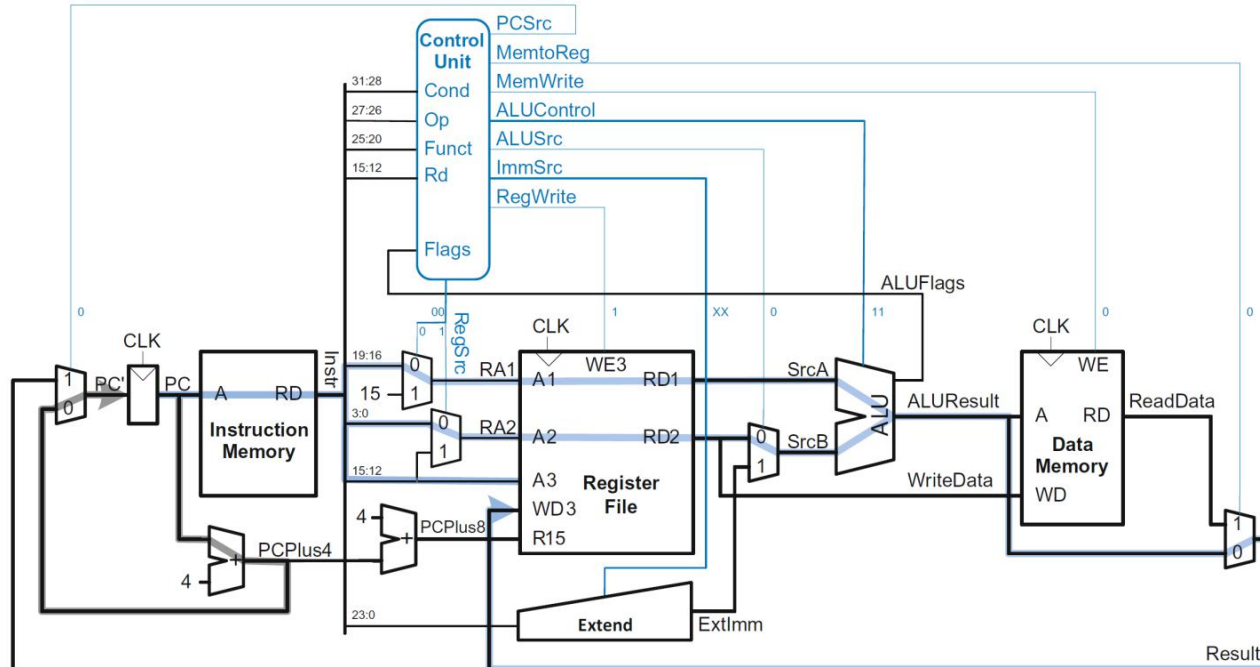

Extended Functionality: CMP


53

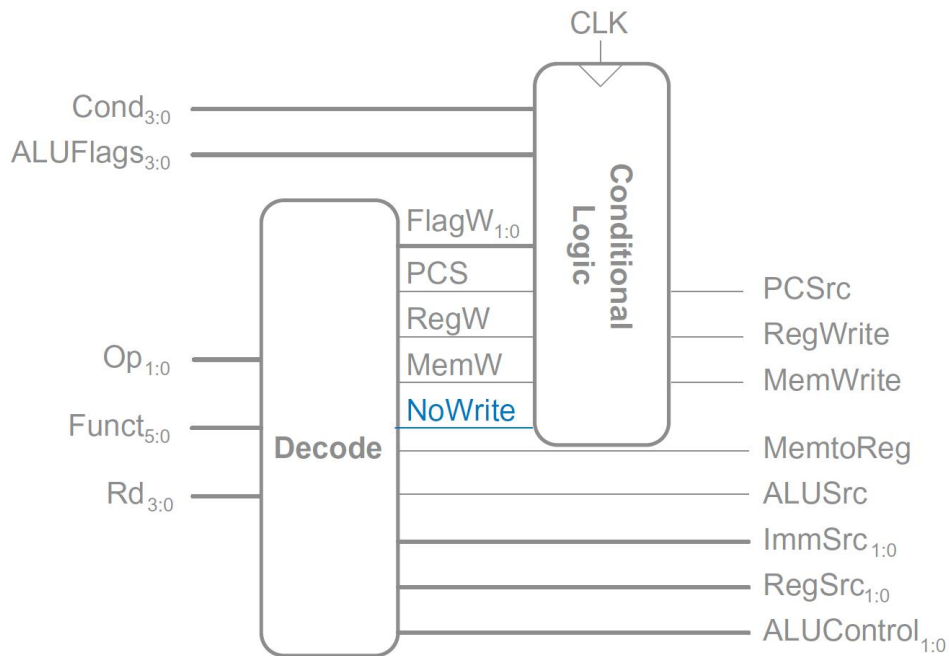

No change to datapath

Extended Functionality: CMP

54

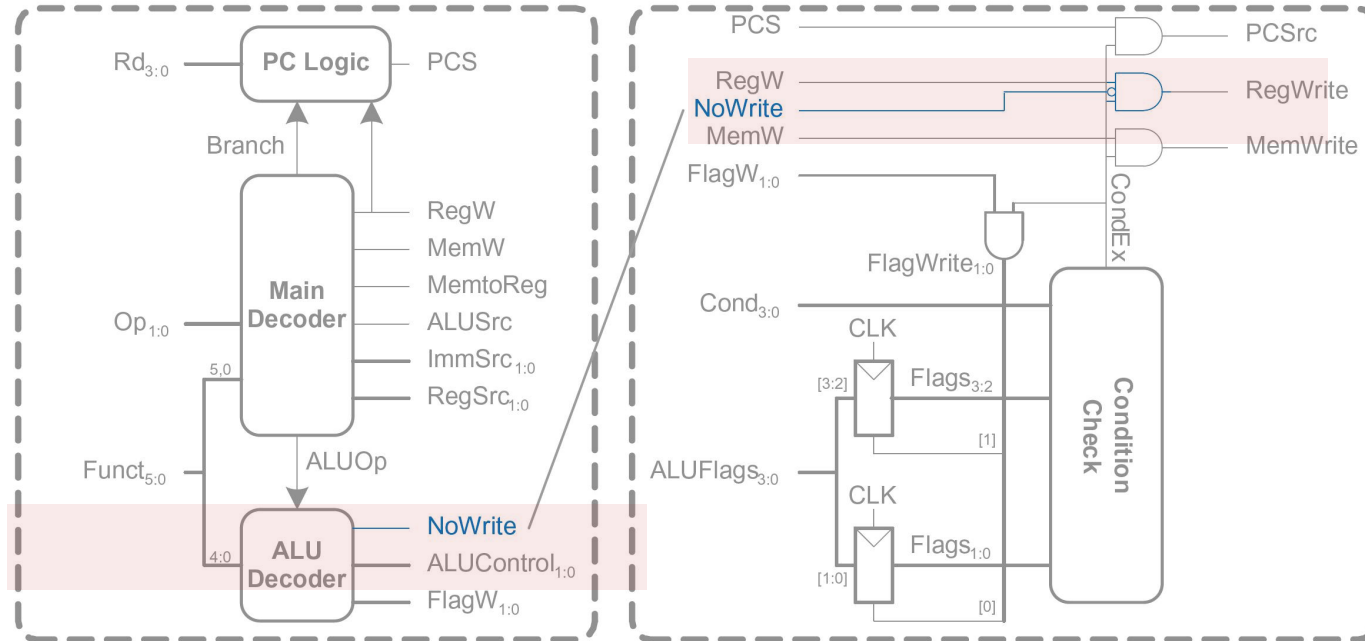



Extended Functionality: CMP

55

ALUOp	Func _{4:1} (cmd)	Func ₀ (S)	Type	ALUControl _{1:0}	FlagW _{1:0}	NoWrite
0	X	X	Not DP	00	00	0
1	0100	0	ADD	00	00	0
		1			11	0
	0010	0	SUB	01	00	0
		1			11	0
	0000	0	AND	10	00	0
		1			10	0
	1100	0	ORR	11	00	0
		1			10	0
	1010	1	CMP	01	11	1


Extended Functionality: Shifted Register

56

 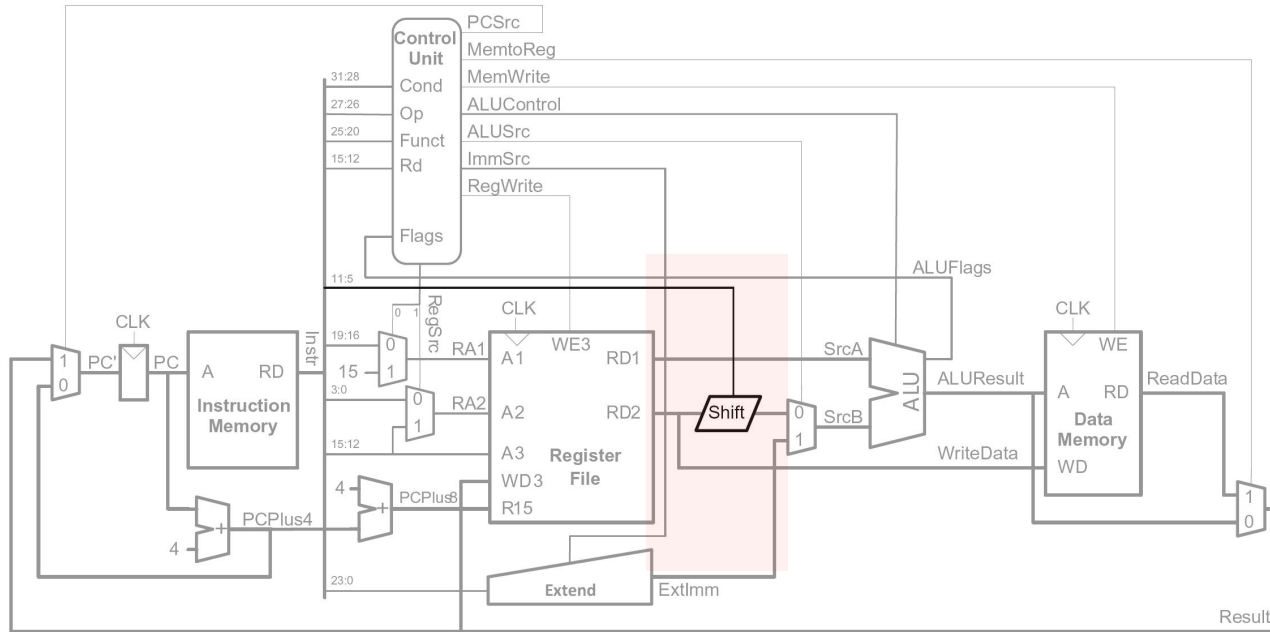

Extended Functionality: Shifted Register

57

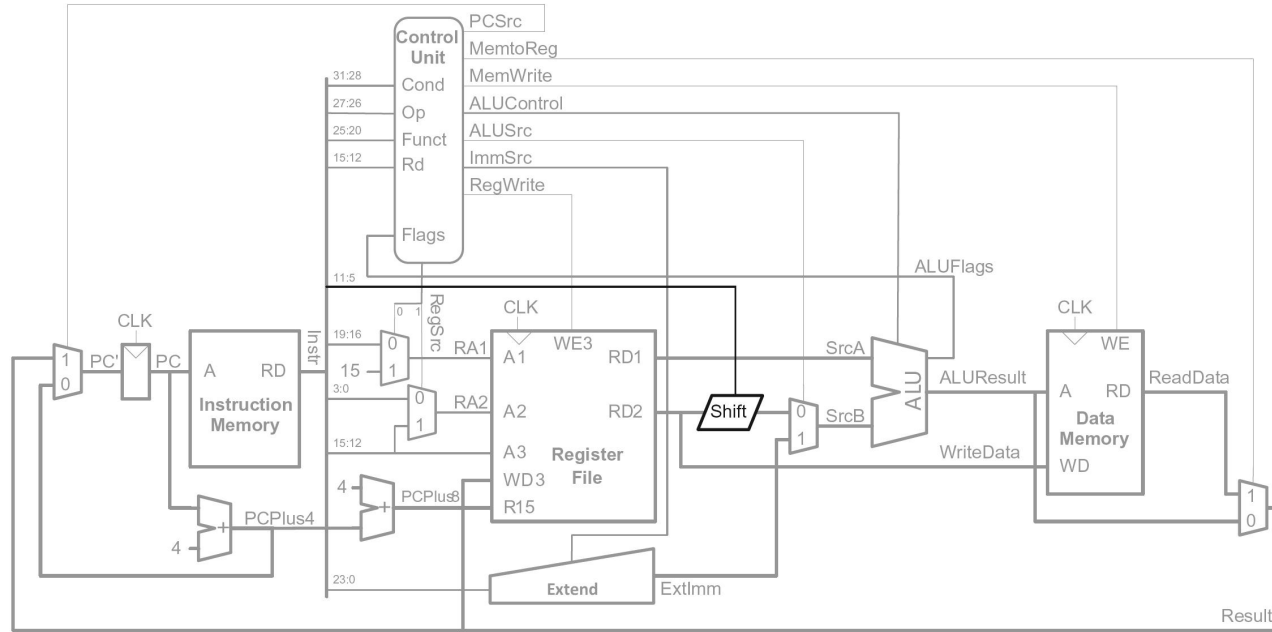

No change to controller

Outline

58

Introduction

Single Cycle Processor

Datapath

Control

Conclusions

Conclusions

59

- We detailed the processor microarchitecture.
- We analyzed the instruction operation and interaction with the processor datapath and control units.
- We conclude that a processor can have different implementations of the ISA based on logic blocks.

Microarchitecture

Computer Architecture



CS3501 – 2024II

PROF.: JGONZALEZ@UTEC.EDU.PE

